

This question paper contains 2 printed pages]

**VA—17—2024**

**FACULTY OF SCIENCE**

**B.Sc. (Third Year) (Sixth Semester) EXAMINATION**

**NOVEMBER/DECEMBER, 2024**

**(CBCS/New Pattern)**

**PHYSICS**

**Paper—XV**

**(Digital and Communication Electronics)**

**(Tuesday, 3-12-2024)**

**Time : 10.00 a.m. to 12.00 noon**

*Time—2 Hours*

*Maximum Marks—40*

**N.B.** :— (i) All questions are compulsory.

(ii) Figures to the right indicate full marks.

(iii) Use of non-programmable calculator is allowed.

1. Define gate. Discuss basic gates with their logic symbols, boolean equations and truth tables. 15

*Or*

(x) Convert the following : 8

(a)  $(598)_{10} = (?)_2$

(b)  $(4AB)_{16} = (?)_{10}$

(c)  $(1101011)_2 = (?)_8$

(d)  $(451)_8 = (?)_2$ .

P.T.O.

- (y) Plot K-map and find out reduced Boolean expression for  
 $f(ABCD) = \sum M(0, 1, 4, 5, 11, 14, 15)$ . 7
2. Define modulation. Obtain an expression for amplitude modulated voltage in terms of modulation index and explain frequency spectrum of A.M. wave. 15
- Or*
- (x) Draw block diagram of superheterodyne radio receiver and explain function of each block. 8
- (y) Discuss linear diode detector with a neat diagram. 7
3. Write short notes on (any two) : 10
- (a) XS-3 code
- (b) Half Adder
- (c) TRF receiver
- (d) Power in A.M.