

This question paper contains **3** printed pages]

**GF—27—2023**

**FACULTY OF SCIENCE AND TECHNOLOGY**

**B.Sc. (CS) (First Semester) EXAMINATION**

**APRIL/MAY, 2023**

**(CBCS/Revised Pattern)**

**COMPUTER SCIENCE**

**Paper BCS-104-B**

**(Fundamentals of Digital Electronics)**

**(Thursday, 27-4-2023)**

**Time : 10.00 a.m. to 1.00 p.m.**

*Time—Three Hours*

*Maximum Marks—75*

*N.B. :—* (i) *All questions are compulsory.*

(ii) *Figures to the right indicate full marks.*

(iii) *Assume suitable data, if required.*

(iv) *Use of any electronic media such as mobile phone, digital diary and electronic calculator is not permitted.*

1. Attempt any *five* of the following (**3** marks each) :

15

(a) Hexadecimal Number System

(b) BCD Code

(c) Two's Complement Binary

(d) Ex-NOR gate

(e) PISO Shift register

(f) Half Adder

(g) Excess-3 Code

P.T.O.

2. Attempt any *three* of the following (5 marks each) :

15

(a) Perform the following conversions :

(i)  $(F53A)_{16} = (?)_8$

(ii)  $(724.2)_8 = (?)_{10}$

(iii)  $(4532)_8 = (?)_2$

(iv)  $(111111101111010)_2 = (?)_{16}$

(v)  $(88)_{10} = (?)_2$

(b) Perform the following operations :

(i)  $(101)_2 + (11100)_2$

(ii)  $(110011)_2 - (1111)_2$

(iii)  $(11)_2 \times (111)_2$

(iv)  $(10100)_2 \div (100)_2$

(v)  $(842)_{10} = (?)_{BCD8421}$

(c) State and prove DeMorgan's first and second theorem.

(d) Explain Decimal and Binary Number Systems in detail.

(e) What is Logic Gate ? Explain NAND and NOR Gates in detail.

3. Attempt any *three* of the following (5 marks each) :

15

(a) Explain SOP and POS forms of Boolean functions in detail.

(b) Explain K-map in detail.

(c) Simplify the following using K-map :

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 8, 9, 10, 11, 14, 15)$$

(d) Express the following Boolean function in its standard or canonical form :

$$Y = A' + BC' + A'BC$$

(e) What is Multiplexer ? Explain 4 : 1 Multiplexer in detail.

4. Attempt any *three* of the following (5 marks each) : 15
- (a) What is Digital to Analog Converter ? Explain any *one* type in detail.
  - (b) What is Counter ? Explain 3 bit synchronous counter in detail.
  - (c) What is flip-flop ? Explain J-K flip-flop in detail.
  - (d) What is Shift Register ? Explain SIPO shift register in detail.
  - (e) What is Decoder ? Explain 2 : 4 Decoder in detail.
5. Write short notes of any *three* of the following (5 marks each) : 15
- (a) T flip-flop
  - (b) Full Adder
  - (c) Octal Number System
  - (d) Gray Code
  - (e) De-multiplexer.